

DigitLabwork#3

Addition/Subtraction/Multiplication/Division in Verilog codes

- [1] Training goals
- [2] Preparations
- [3] Lab-task instruction
- [4] Observations/Evaluation

=====

[1] Training goals

Through the lab-work, class members are expected to get acquainted with the following matters.

- a)) operation of circuits doing addition, subtraction, multiplication and division;
- b)) the use of Verilog for logic circuit description and simulation, including
 - ** circuit module building up in Verilog,
 - ** setting up of the test data;
- c)) the interactive commands required in operating the Verilog-code development system:
 - ** compilation for a syntax error-free Verilog description and test data set;
 - ** simulation of the Verilog-coded circuit module;
 - [** synthesis of the Verilog-coded circuit module].

[2] Preparation

Every class member should get oneself prepared by studying the following materials prior to attending the lab-work sessions.


- a)) Refer to “Digital Circuits 123”-section[1] and, better yet, datasheets from IC manufacturers such that functional/electrical/timing specifications regarding the circuit components targeted in the lab-work are understood;
- b)) Refer to “Digital Circuits 123”-section [4], where examples of Verilog-coding of the circuit components targeted in the lab-work are offered;
- c)) Refer to “Digital Circuits 123”-section [4] so as to know about how test data for circuit simulation should be arranged;
- d)) Refer to “Development Context of Verilog Code” for operational details in running the developing system.

[3] Lab-task instruction

In digitlabwork#3, 3 tasks are assigned to every class members as given below.

[TASK1]

 - (1) Write a Verilog code for an 8bit adder in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals

a)) coding specifications:

- ** write 3 modules of 8bit adders in gate-level, dataflow-level and behavior-level descriptions, respectively.
- ** the 3 modules will share the same A,B and C_{in} inputs, and each generates respective SUM and C_o outputs.
- ** write Verilog codes for generating test data sequence as requested.

b)) circuit specifications:

```

** I/O layout:      3 input sets      A[7:0],
                                     B[7:0],
                                     Cin;
                    outputs            SUM[7:0],
                                     Co;

```


**** Functional:**

A	B	C _{in}	SUM	C _o
1s/0s	1s/0s	1/0	A+B+C _{in}	(A[7]&B[7]) (A[7]&C ₆) (B[7]&C ₆)

**** Timing:** no delay(s) to be considered in this task


c)) testing data:

[test case 1]

 

[TASK2]

 - (1) Write a Verilog code for a circuit capable of doing 8bit subtraction in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals

a)) coding specifications:

- ** B is the data to be subtracted from A, A-B that is,
- ** using an 8bit adder as the underlying component is recommended,
- ** write 3 modules of 8bit subtraction circuit in gate-level, dataflow-level and behavior-level descriptions, respectively.
- ** the 3 modules will share the same A, B and carry inputs, and each generates respective difference and carry outputs.
- ** write Verilog codes for generating test data sequence as requested.

b)) circuit specifications:

- ** I/O layout: 3 input sets A[7:0], B[7:0],


output $C_{in};$
 $DIFF[7:0],$
 $C_o;$

**** Functional:**

			$B2C = \sim B + 1$	
A	B	C_{in}	DIFF	C_o
1s/0s	1s/0s	1/0	$A + B2C + C_{in}$	$(A[7] \& B2C[7]) $ $(A[7] \& C_6) $ $(B2C[7] \& C_6)$

**** Timing:** no delay(s) to be considered in this task


c) testing data:

 

**** the testing stops at time-unit 130;**

[TASK3]

 - (1) Write a Verilog code for 8bit x 8bit unsigned multiplication in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals

a) coding specifications:

**** multiplication done either by iterative/successive additions or by**

```

** try not using a statement like Po=A*B in behavior-level description;
   coding in a way that more or less shows the procedure about how
   the multiplication being done, instead,
** write 3 modules of 8bit unsigned multiplier in gate-level,
   dataflow-level and behavior-level descriptions, respectively.
** the 3 modules will share the same A,B inputs, and each comes out
   with respective product.
** write Verilog codes for generating test data sequence as requested.

```

```

** I/O layout:      2 input sets      A[7:0],
                                   B[7:0];
                   output      P[15:0];

```

A	B	P
1s/0s	1s/0s	AxB

The diagram illustrates two horizontal timelines, A and B, with vertical dashed lines indicating time points. The x-axis is labeled 't' with values 0, 5, 15, 22, 35, 50, 70, 75, 95, 115, 120, 130.


Timeline A (top) has labels: 88H, FFH, 12H, 28H, 74H, 29H, 5AH.

Timeline B (bottom) has labels: 22H, 77H, 66H, D5H, FEH.

**** the testing stops at time-unit 130;**

[TASK4]

 - (1) Write a Verilog code for 8bit/8bit unsigned division in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals

a)) coding specifications:

- ** use iterative/successive subtraction as the underlying dividing mechanism, unless you know otherwise how the division could be done more elegantly,
- ** try not using a statement like $Q=A/B$ in behavior-level description; coding in a way that more or less shows the procedure about how the division being done instead,
- ** write 3 modules of 8bit unsigned divider in gate-level, dataflow-level and behavior-level descriptions, respectively.
- ** the 3 modules will share the same A,B inputs, and each comes out respective quotient and remainder.
- ** write Verilog codes for generating test data sequence as requested.

b)) circuit specifications:

- ```

** I/O layout: 2 input sets A[7:0],
 B[7:0];
 output Q[7:0];
 R[7:0]

```


**\*\* Functional:**

|       |       |                  |
|-------|-------|------------------|
| A     | B     | Q,R              |
| 1s/0s | 1s/0s | $A=B \times Q+R$ |

- \*\* Timing:** no delay(s) to be considered in this task

**c)) testing data:**

```
[test case 1]
```

 

#### [4] Observations/Evaluation

- Try deriving fast carry  $C_6, C_5, C_4, C_3, C_2, C_1, C_0$  in terms of  $A_6, A_5, A_4, A_3, A_2, A_1, A_0$  and  $B_6, B_5, B_4, B_3, B_2, B_1, B_0$ , and then ask oneself:
  - \*\* for any  $C_j$ , which part of A and B are involved if logic-level of the carry generating circuit is to be limited under, say, no more than 3?
  - \*\* what does one see regarding the logic gates required for  $C_j$  generation as j getting higher?
- While observing the operation of subtracting circuit, tell about the implication of seeing and not seeing  $C_o$  generation, respectively.
- If, besides DIFF and  $C_o$ , a third output  $O_{\text{verflow}}$  is needed while using 2 8bit subtraction modules for 16bit subtraction, what should be done?
- Dealing with iterative addition for adding up partial products during multiplication would seem require a sequential module. So is the multiplier combinational or sequential? What about the divider if iterative-subtraction being deployed inside?
- What more are to be done if multiplier/divider for signed integers is desired?
- Difficulties encountered while working on the assigned tasks may more or less reflect one's deficiency in one or more aspects of the following:
  - \*\* experiences on the circuit structures and operations of the three basic modules which are building blocks deployed in all digital systems;
  - \*\* experiences on the mastery of Verilog and the tools of the developing environment;
  - \*\* readiness for the lab-task at hand.

Inexperience won't be a problem, as it fades away eventually when one pours in time and dedication; whereas the third would present a serious issue. The

so called “poor-luck-in-the-laboratory” would persist, by which one will always be haunted as long as the unsound attitude continues.

g)) It’s expected that, after DigitLabwork#3, one should feel confident, or at least comfortable, in dealing with circuit doing addition, subtraction, multiplication and division using Verilog. Hopefully this is the case of everyone in the class.