

DigitLabwork#2

MUX/DEMUX/Parity-Check in Verilog codes

- [1] Training goals
- [2] Preparations
- [3] Lab-task instruction
- [4] Observations/Evaluation

=====

[1] Training goals

Through the lab-work, class members are expected to get acquainted with the following matters.

- a)) the functions of MUXs, DEMUXs and parity-check circuits;
- b)) the use of Verilog for logic circuit description and simulation, including
 - ** circuit module building up in Verilog,
 - ** setting up of the test data;
- c)) the interactive commands required in operating the Verilog-code development system:
 - ** compilation for a syntax error-free Verilog description and test data set;
 - ** simulation of the Verilog-coded circuit module;
 - [** synthesis of the Verilog-coded circuit module].

[2] Preparation

Every class member should get oneself prepared by studying following materials prior to attending the lab-work sessions.


- a)) Refer to “Digital Circuits 123”-section[1] and, better yet, datasheets from IC manufacturers such that functional/electrical/timing specifications regarding the circuit components targeted in the lab-work are understood;
- b)) Refer to “Digital Circuits 123”-section [4], where examples of Verilog-coding of the circuit components targeted in the lab-work are offered;
- c)) Refer to “Digital Circuits 123”-section [4] so as to know about how test data for circuit simulation should be arranged;
- d)) Refer to “Development Context of Verilog Code” for operational details in running the developing system.

[3] Lab-task instruction

In digitlabwork#2, 3 tasks are assigned to every class members as given below.

[TASK1]

 - (1) Write a Verilog code for an 8to1 multiplexer with \overline{EN} control and tri-state output in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals

a)) coding specifications:

- ** write 3 modules of 8to1 multiplexer in gate-level, dataflow-level and behavior-level descriptions, respectively.
- ** the 3 modules will share the same inputs of data channels and controls, and each operates with respective 1-bit outputs.
- ** write Verilog codes for generating test data sequence as requested.

b)) circuit specifications:

- ** I/O layout: 3 input sets $D_7D_6D_5D_4D_3D_2D_1D_0$,
 sel_2 - sel_0 ,
 \overline{EN} ;
output Y_o ;


** Functional:

\overline{EN}	$D_7 \sim D_0$	sel_2	sel_1	sel_0	Y_o
0	X	X			Z
1	X	0	0	0	D_0
		0	0	1	D_1
		0	1	0	D_2
		0	1	1	D_3
		1	0	0	D_4
		1	0	1	D_5
		1	1	0	D_6
		1	1	1	D_7

- ** Timing: no delay(s) to be considered in this task

c) testing data:


[test case 1]

 

** the testing stops at time-unit 130;

** determine the switching time instants for \overline{EN} according to the waveform shown above.

[test case 2]

 


** the testing stops at time-unit 130;

** determine the switching time instants for \overline{EN} according to the waveform shown above.

[TASK2]

 - (1) Write a Verilog code for an 1to8 demultiplexer with \overline{EN} control and tri-state output in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms

of output signals

a)) coding specifications:

**** write 3 modules of 1to8 demultiplexer in gate-level, dataflow-level and behavior-level descriptions, respectively.**

**** the 3 modules will share the same inputs of data channel and controls, and each operates with respective 8-bit outputs.**

**** write Verilog codes for generating test data sequence as requested.**

b)) circuit specifications:

**** I/O layout:**

3 input sets	D _{in} ,
	sel ₂ -sel ₀ ,
	<u>EN</u> ;
output	Y ₇ Y ₆ Y ₅ Y ₄ Y ₃ Y ₂ Y ₁ Y ₀ ;


**** Functional:**

$\overline{\text{EN}}$	D _{in}	sel ₂		sel ₂	sel ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀	
0	X	X				Z	Z	Z	Z	Z	Z	Z	Z	
1	X	0	0	0	Z	Z	Z	Z	Z	Z	Z	D _{in}	Z	
		0	0	1						D _{in}	D _{in}			
		0	1	0					D _{in}		Z	Z		
		0	1	1					D _{in}	Z				
		1	0	0				D _{in}						Z
		1	0	1										
		1	1	0							D _{in}	Z		
		1	1	1					D _{in}	Z				

**** Timing:** no delay(s) to be considered in this task

c)) testing data:


[test case 1]

 

```
** the testing stops at time-unit 130;
```

** determine the switching time instants for \overline{EN} according to the waveform shown above.

[test case 2]

 


** the testing stops at time-unit 130;

** determine the switching time instants for \overline{EN} according to the waveform shown above.

[TASK3]

 - (1) Write a Verilog code for an 8bit parity checking circuit in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals

a)) coding specifications:

- ** write 3 modules of 8bit parity indicator in gate-level, dataflow-level and behavior-level descriptions, respectively.
- ** the 3 modules will share the same inputs of data channels and controls, and each operates with respective 1-bit outputs.
- ** write Verilog codes for generating test data sequence as requested.

b)) circuit specifications:

- ** I/O layout: 3 input sets $D_7D_6D_5D_4D_3D_2D_1D_0$,
 chk_1chk_0 ,
 $\overline{even/odd}$;

output Y_o ;


**** Functional:**

even/ $\overline{\text{odd}}$	D_{in}	chk_1	chk_0	Y_o
0	X	0	0	L-half odd
		0	1	Even-bit odd
		1	0	Odd-bit odd
		1	1	full 8bit odd
1	X	0	0	L-half even
		0	1	Even-bit even
		1	0	Odd-bit even
		1	1	full 8bit even


**** Timing:** no delay(s) to be considered in this task

c) testing data:

[test case 1]

 

[test case 2]

 

**** D_{in} :** repetitively varies from 00H to FFH, each pattern remains 1 time-unit;

**** determine your own switching of even/odd and sel[1:0] after time-unit 130.**

[4] Observations/Evaluation

a)) Difficulties encountered while working on the assigned tasks may more or less reflect one's deficiency in one or more aspects of the following:

- ** experiences on the circuit structures and operations of the three basic modules which are building blocks deployed in all digital systems;
- ** experiences on the mastery of Verilog and the tools of the developing environment;
- ** readiness for the lab-task at hand.

Inexperience won't be a problem, as it fades away eventually when one pours in time and dedication; whereas the third would present a serious issue. The so called "poor-luck-in-the-laboratory" would persist, by which one will always be haunted as long as the unsound attitude continues.

b)) It's expected that, after DigitLabwork#2, one should feel confident, or at least comfortable, in dealing with circuit structures and operations of MUXs, DEMUXs, and parity-check circuits using Verilog. Hopefully this is the case of everyone in the class.