

DigitLabwork#4

Shift-register and Counter in Verilog codes

- [1] Training goals
- [2] Preparations
- [3] Lab-task instruction
- [4] Observations/Evaluation

= = = = =

[1] Training goals

Through the lab-work, class members are expected to get acquainted with the following matters.

- a)) operation of left-/right-shift registers and counters;
- b)) the use of Verilog for logic circuit description and simulation, including
 - ** circuit module building up in Verilog,
 - ** setting up of the test data;
- c)) the interactive commands required in operating the Verilog-code development system:
 - ** compilation for a syntax error-free Verilog description and test data set;
 - ** simulation of the Verilog-coded circuit module;
 - [** synthesis of the Verilog-coded circuit module].

[2] Preparation

Every class member should get oneself prepared by studying the following materials prior to attending the lab-work sessions.


- a)) Refer to “Digital Circuits 123”-section[1] and, better yet, datasheets from IC manufacturers such that functional/electrical/timing specifications regarding the circuit components targeted in the lab-work are understood;
- b)) Refer to “Digital Circuits 123”-section [4], where examples of Verilog-coding of the circuit components targeted in the lab-work are offered;
- c)) Refer to “Digital Circuits 123”-section [4] so as to know about how test data for circuit simulation should be arranged;
- d)) Refer to “Development Context of Verilog Code” for operational details in running the developing system.

[3] Lab-task instruction

In digitlabwork#4, 2 tasks are assigned to every class members as given below.

[TASK1]

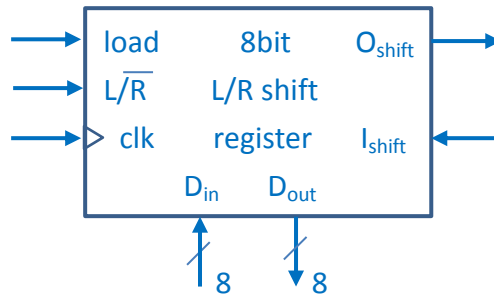- (1) Write a Verilog code for an 8bit shift register with general controls in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals
- (3) Try drawing the circuit diagram of the 8bit shift register, using 1bit D-reg, logic gates and components one deems as necessary.

a)) coding specifications:

- ** write behavior-level descriptions for the 8bit L/R shift-register.
- ** the module has load, L/R, clk, D_{in}, and I_{shift} as inputs, and D_{out} and O_{shift} as outputs.
- ** write Verilog codes for generating test data sequence as requested.

b)) circuit specifications:

- ```

** I/O layout: 5 input sets Din[7:0],
 load, L/R, clk, Ishift;
 outputs Dout[7:0],
 Oshift;


```

**\*\* Functional:**

| load | clk | L/R | I <sub>shift</sub> | D <sub>in</sub> | O <sub>shift</sub>   | D <sub>out</sub>                                                                                     |
|------|-----|-----|--------------------|-----------------|----------------------|------------------------------------------------------------------------------------------------------|
| 1    | x   | x   | x                  | 1s/0s           | x                    | D <sub>in</sub>                                                                                      |
| 0    | ↑   | 1   | 1/0                | x               | D <sub>out</sub> [7] | D <sub>out</sub> [j] = D <sub>out</sub> [j-1],    j:7~1<br>D <sub>out</sub> [0] = I <sub>shift</sub> |
|      |     | 0   | 1/0                | x               | D <sub>out</sub> [0] | D <sub>out</sub> [j] = D <sub>out</sub> [j+1],    j:6~0<br>D <sub>out</sub> [7] = I <sub>shift</sub> |

- \*\* Timing:** no delay(s) to be considered in this task

c) testing data:

 


\*\* the testing stops at time-unit 273;

\*\* D<sub>in</sub> changes at 2 time-unit after the falling edge of **clk**;

\*\* derive unspecified timing instances using information revealed in the chart whenever necessary.

**[TASK2]**

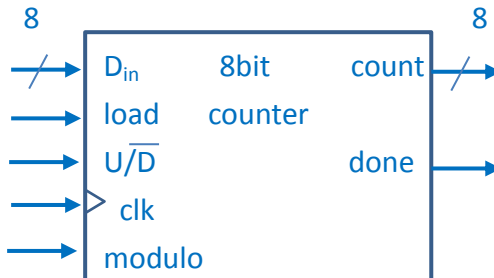- (1) Write a Verilog code for an 8bit counter with general controls in compliance with the requirements given below.



- (2) Put the codes under simulation; observe and interpret the waveforms of output signals
- (3) Try drawing the circuit diagram of the 8bit shift register, using 1bit D-reg, logic gates and components one deems as necessary.

**a)) coding specifications:**

- \*\* write behavior-level descriptions for the 8bit counter in question.
- \*\* the module has  $D_{in}$ , load,  $\overline{U/D}$ , clk, modulo as inputs, and count and done as outputs.
- \*\* write Verilog codes for generating test data sequence as requested.

**b)) circuit specifications:**

- ```

** I/O layout:   input sets   Din[7:0],
                  load, U/D, clk, modulo;

                  outputs      count[7:0],
                               done;

```

**** Functional:**

load	clk	$\overline{U/D}^*$	D_{in}	mod*	c_end*	count	done
1	↑	1	1s/0s	0	0FFH	D_{in}^*	0
1	↑	0	1s/0s	0	0H	D_{in}^*	0
1	↑	1	1s/0s	1	D_{in}^*	0	0
1	↑	0	1s/0s	1	0H	D_{in}^*	0
0	↑	1	x	0	c_end*	count++	if count==c_end* { count= D_{in}^* ; done=1; } else done=0;

0	↑	0	x	0	c_end*	count--	if count==0 { count=D _{in} *; done=1; } else done=0;
0	↑	1	x	1	c_end*	count++	if count==c_end* { count=0; done=1; } else done=0;
0	↑	0	x	1	c_end*	count--	if count==c_end* { count=D _{in} *; done=1; } else done=0;

[note] ** modulo: 0 for binary counting
from D_{in} to 0FFH for U/ \overline{D} ==1
D_{in} to 0H for U/ \overline{D} ==0

1 for decimal counting
from 0 to D_{in} for U/D==1
D_{in} to 0H for U/ \overline{D} ==0

** mod*: internal copy of modulo

** U/ \overline{D} *: internal copy of $\overline{U/D}$


** D_{in}*: internal copy of D_{in} or 0 as the initial value of counting operation;


** c_end*: internal copy of 0H, 0FFH, or D_{in} as the ending value of counting;

** internal copies of input signals are set at clk rising edge.

** Timing: no delay(s) to be considered in this task

c) testing data:

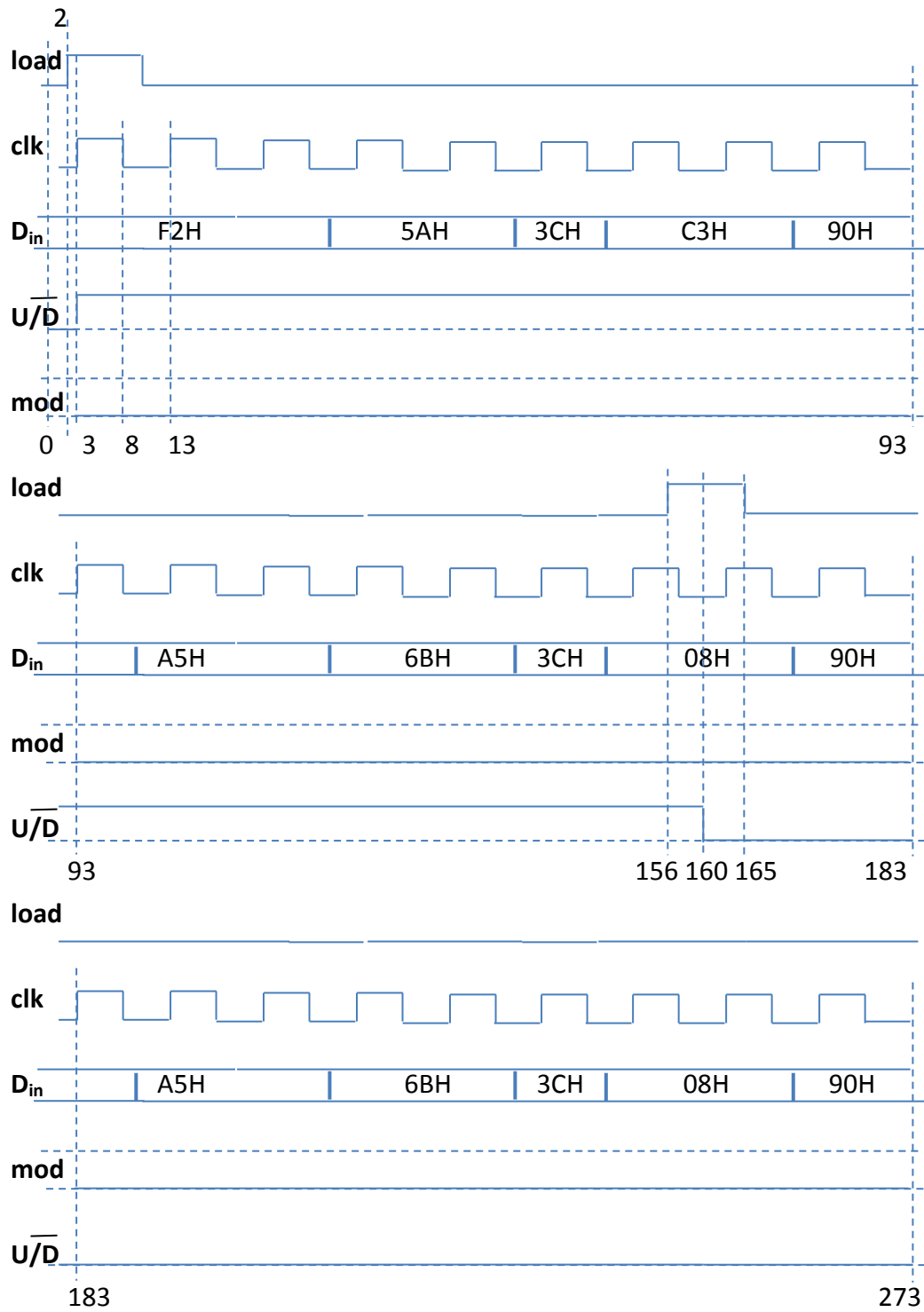

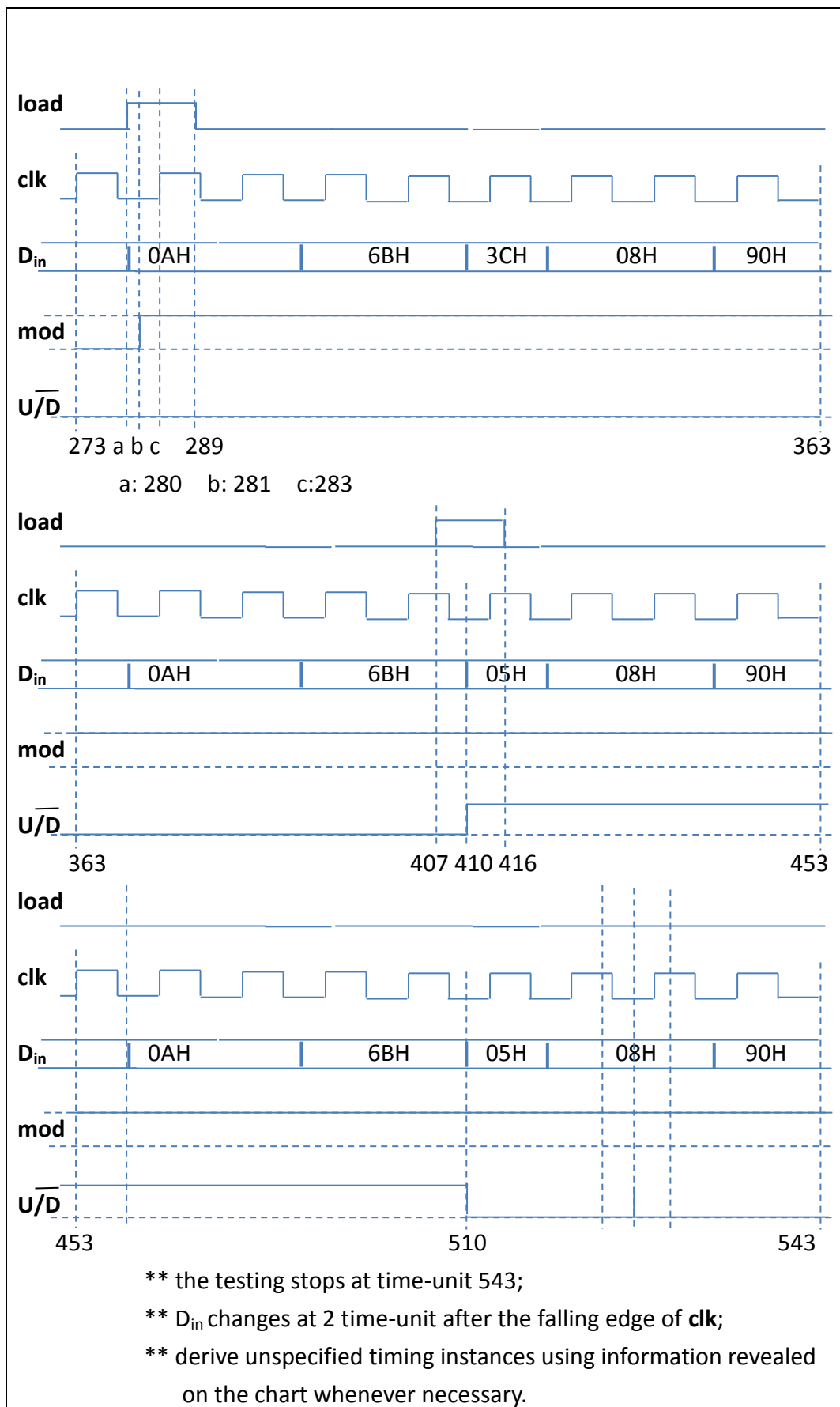

[4] Observations/Evaluation

- a)) What would the shift register respond if D_{in} varied when **load** is high? (as indicated by the 2nd **load** in the testing sequence)
- b)) What would be shift register respond if L/\overline{R} switching occurred at shifting?
- c)) In the function spec. of the 8bit counter, it is noted that inputs are strobed for internal copies at the rising edge of the clock when **load** is high.
- ** Could you think of any undesired situations which might occur at counting if there are no internal copies of $\overline{U/D}$, and D_{in} made available while **load** is in effect?
 - ** While making internal copies of modulo, $\overline{U/D}$, and D_{in} at load-phase, the copying is triggered by $clk \uparrow$ as noted in the function table. Is it possible making internal copies by using **load** alone without causing any undesired consequence?
- d)) Difficulties encountered while working on the assigned tasks may more or less reflect one's deficiency in one or more aspects of the following:
- ** experiences on the circuit structures and operations of the three basic modules which are building blocks deployed in all digital systems;
 - ** experiences on the mastery of Verilog and the tools of the developing environment;
 - ** readiness for the lab-task at hand.
- Inexperience won't be a problem, as it fades away eventually when one pours in time and dedication; whereas the third would present a serious issue. The so called "poor-luck-in-the-laboratory" would persist, by which one will always be haunted as long as the unsound attitude continues.
- e)) It's expected that, after DigitLabwork#4, one should feel confident, or at least comfortable, in dealing with shifters and counters using Verilog. Hopefully this is the case of everyone in the class.